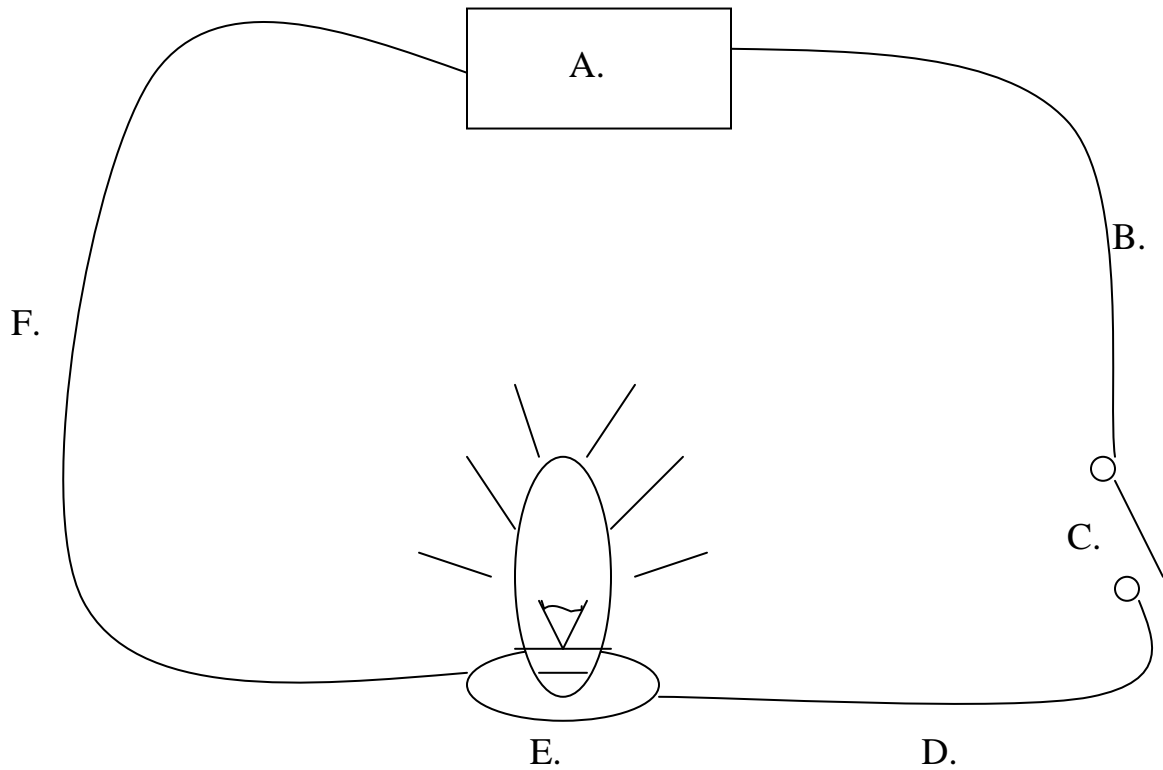


Name \_\_\_\_\_ Date \_\_\_\_\_

# Circuit



Use the following terms to identify A-F:

Switch

Conductor

Power Source

Load

Conductor

Conductor

A. \_\_\_\_\_

D. \_\_\_\_\_

B. \_\_\_\_\_

E. \_\_\_\_\_

C. \_\_\_\_\_

F. \_\_\_\_\_