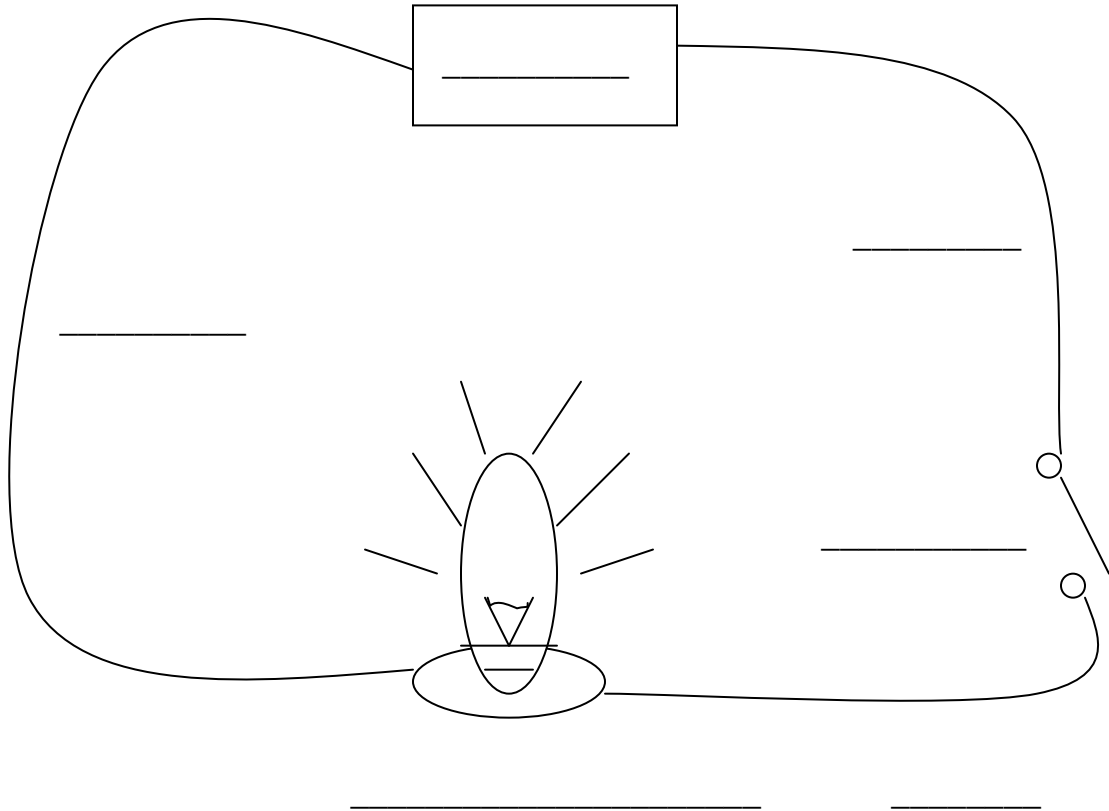


Name _____ Date _____

Circuit



Label the picture above with the following parts of a circuit.

- Power Source
- Switch
- Load
- Conductor
- Conductor
- Conductor